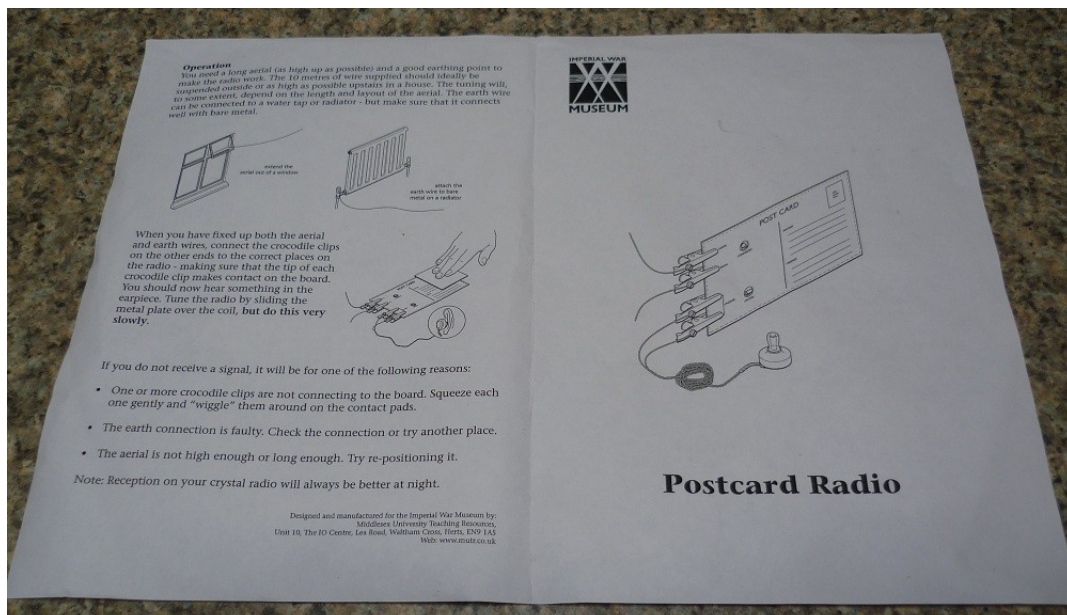


Post Card Radio Kit – page 1

I bought this as a kit from the Imperial War Museum in London when I was there in July 2011, could not resist it.



It is a very simple crystal set and tuning is via the metal plate supplied with the kit, you just slide it over the printed circuit coil to vary the tuning capacitance, very neat idea.



The instructions are brief but adequate to enable even someone new to radio technology to assemble the kit. The kit is complete with a crystal earphone, antenna and earth wires and alligator clips for making the connections. A detector diode and RF filter capacitor are already soldered to the circuit board.

Post Card Radio Kit – page 2

